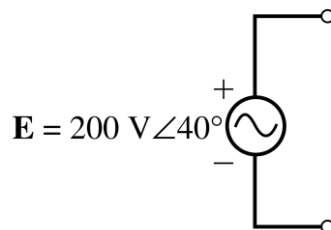


## Sheet (11)


### Q1:- Answer the following questions

- Convert each of the following to polar form:
  - $5 + j12$
  - $9 - j6$
  - $-8 + j15$
  - $-10 - j4$
- Convert each of the following to rectangular form:
  - $6\angle 30^\circ$
  - $14\angle 90^\circ$
  - $16\angle 0^\circ$
  - $6\angle 150^\circ$
  - $20\angle -140^\circ$
  - $-12\angle 30^\circ$
  - $-15\angle -150^\circ$
- Plot each of the following on the complex plane:
  - $4 + j6$
  - $j4$
  - $6\angle -90^\circ$
  - $10\angle 135^\circ$
- Simplify the following using powers of j:
  - $j(1 - j1)$
  - $(-j)(2 + j5)$
  - $j[j(1 + j6)]$
  - $(j4)(-j2 + 4)$
  - $(2 + j3)(3 - j4)$
  - $(-2 - j3)(3 - j4)$
- Add or subtract as indicated. Express your answer in rectangular form.
  - $(4 + j8) + (3 - j2)$
  - $(4 + j8) - (3 - j2)$
  - $(4.1 - j7.6) + 12\angle 20^\circ$
  - $2.9\angle 25^\circ - 7.3\angle -5^\circ$
  - $9.2\angle -120^\circ - (2.6 + j4.1)$
- Multiply or divide as indicated. Express your answer in polar form.
  - $(37 + j9.8)(3.6 - j12.3)$
  - $(41.9\angle -80^\circ)(16 + j2)$
  - $(42 + j18.6)/(19.1 - j4.8)$
  - $(42.6 + j187.5)/(11.2\angle 38^\circ)$
- Reduce each of the following to polar form:
  - $15 - j6 - \left[ \frac{18\angle 40^\circ + (12 + j8)}{11 + j11} \right]$
  - $\frac{21\angle 20^\circ - j41}{36\angle 0^\circ + (1 + j12) - 11\angle 40^\circ}$
  - $\frac{18\angle 40^\circ - 18\angle -40^\circ}{7 + j12} - \frac{16 + j17 + 21\angle -60^\circ}{4}$
- In the manner of the following figure, represent each of the following as transformed sources.
  - $e = 100 \sin(\omega t + 30^\circ) \text{ V}$
  - $e = 15 \sin(\omega t - 20^\circ) \text{ V}$
  - $e = 50 \sin(\omega t + 90^\circ) \text{ V}$
  - $e = 50 \cos \omega t \text{ V}$
  - $e = 40 \sin(\omega t + 120^\circ) \text{ V}$
  - $e = 80 \sin(\omega t - 70^\circ) \text{ V}$




Transformed source

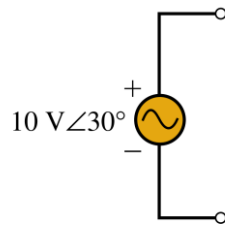9. Determine the sinusoidal equivalent for each of the transformed sources of the following figure




(a)

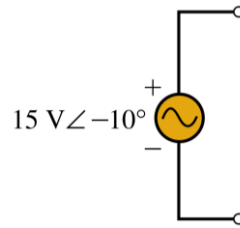


(b)

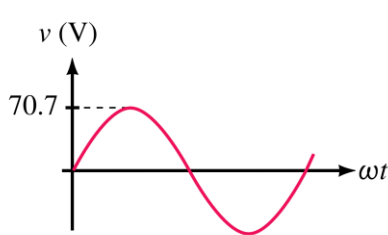
10. Given:  $e_1 = 10 \sin(\omega t + 30^\circ)$  V and  $e_2 = 15 \sin(\omega t - 20^\circ)$  V. Determine their sum  $v = e_1 + e_2$
- Convert  $e_1$  and  $e_2$  to phasor form.
  - Determine  $V = E_1 + E_2$ .
  - Convert  $V$  to the time domain.
  - Sketch  $e_1$ ,  $e_2$ , and  $v$ .
11. Repeat Problem 10 for  $v = e_1 - e_2$ .
12. Express the voltages and currents of the following figure as time domain and phasor domain quantities.




(a)

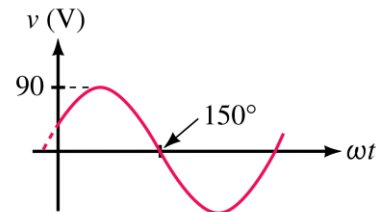

(b)

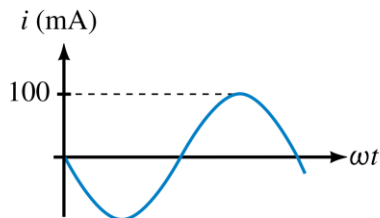


(c)

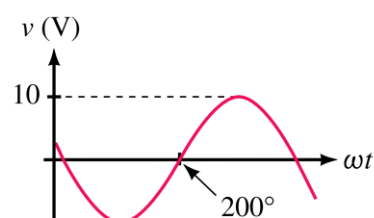


(d)

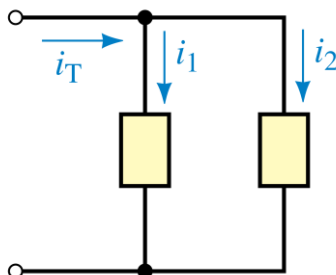
13. For the following figure,  $i_1 = 25 \sin(\omega t + 36^\circ)$  mA and  $i_2 = 40 \cos(\omega t - 10^\circ)$  mA.
- Determine phasors  $I_1$ ,  $I_2$  and  $I_T$ .
  - Determine the equation for  $i_T$  in the time domain.



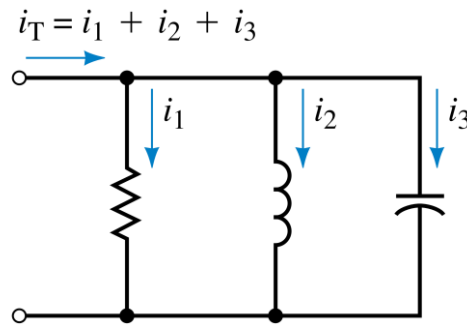
14. For the figure of problem (13),  $i_T = 50 \sin(\omega t + 60^\circ)$  A and  $i_2 = 20 \sin(\omega t - 30^\circ)$  A.
- Determine phasors  $I_T$  and  $I_2$ .
  - Determine  $I_1$ .
  - From (b), determine the equation for  $i_1$ .
15. For following figure,  $i_1 = 7 \sin \omega t$  mA,  $i_2 = 4 \sin (\omega t - 90^\circ)$  mA, and  $i_3 = 6 \sin (\omega t + 90^\circ)$  mA.
- Determine phasors  $I_1, I_2, I_3$  and  $I_T$ .
  - Determine the equation for  $i_T$  in the time domain.



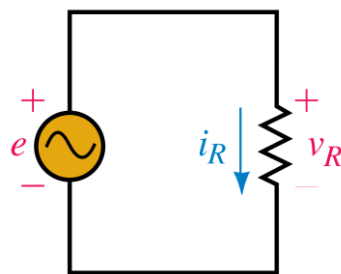16. For the following figure,  $R = 12 \Omega$ . For each of the following, determine the current or voltage and sketch.
- $v = 120 \sin \omega t$  V,  $i = \dots\dots\dots$
  - $v = 120 \sin (\omega t + 27^\circ)$  V,  $i = \dots\dots\dots$
  - $i = 17 \sin (\omega t - 56^\circ)$  mA,  $v = \dots\dots\dots$
  - $i = -17 \cos(\omega t - 67^\circ)$  mA,  $v = \dots\dots\dots$




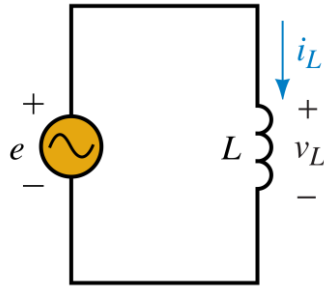17. Given  $v = 120 \sin (\omega t + 52^\circ)$  V and  $i = 15 \sin (\omega t + 52^\circ)$  mA, what is  $R$ ?
18. Two resistors  $R_1 = 10 \text{ k}\Omega$  and  $R_2 = 12.5 \text{ k}\Omega$  are in series. If  $i = 14.7 \sin(\omega t + 39^\circ)$  mA,
- What are  $v_{R1}$  and  $v_{R2}$ ?
  - Compute  $v_T = v_{R1} + v_{R2}$  and compare to  $v_T$  calculated from  $v_T = i R_T$ .
19. The voltage across a certain component is  $v = 120 \sin(\omega t + 55^\circ)$  V and its current is  $-18 \cos(\omega t + 145^\circ)$  mA. Show that the component is a resistor and determine its value.
20. For the following figure,  $V_m = 10$  V and  $I_m = 5$  A. For each of the following, determine the missing quantity:
- $v_L = 10 \sin(\omega t + 60^\circ)$  V,  $i_L = \dots\dots\dots$
  - $v_L = 10 \sin(\omega t - 15^\circ)$  V,  $i_L = \dots\dots\dots$
  - $i_L = 5 \cos(\omega t - 60^\circ)$  A,  $v_L = \dots\dots\dots$
  - $i_L = 5 \sin(\omega t + 10^\circ)$  A,  $v_L = \dots\dots\dots$




21. What is the reactance of a 0.5-H inductor at
  - a. 60 Hz
  - b. 1000 Hz
  - c. 500 rad/s
22. For the figure of problem (20),  $e = 100 \sin \omega t$  and  $L = 0.5$  H. Determine  $i_L$  at
  - a. 60 Hz
  - b. 1000 Hz
  - c. 500 rad/s
23. For the figure of problem (20), let  $L = 200$  mH.
  - a. If  $v_L = 100 \sin 377t$  V, what is  $i_L$  ?
  - b. If  $i_L = 10 \sin(2\pi \times 400t - 60^\circ)$  mA, what is  $v_L$ ?
  - c.  $v_L = 40 \sin(\omega t + 30^\circ)$  V,  $i_L = 364 \sin(\omega t - 60^\circ)$  mA, and  $L = 2$  mH, what is  $f$ ?
  - d.  $i_L = 250 \sin(\omega t + 40^\circ)$  mA,  $v_L = 40 \sin(\omega t + \theta)$  V, and  $f = 500$  kHz, what are  $L$  and  $\theta$  ?
24. For the following figure,  $V_m = 10$  V and  $I_m = 5$  A. For each of the following, determine the missing quantity:
 

a. $v_C = 10 \sin(\omega t + 60^\circ)$ V,	$i_C = \dots\dots\dots$
b. $v_C = 10 \sin(\omega t - 15^\circ)$ V,	$i_C = \dots\dots\dots$
c. $i_C = 5 \cos(\omega t - 60^\circ)$ A,	$v_C = \dots\dots\dots$
d. $i_C = 5 \sin(\omega t + 10^\circ)$ A,	$v_C = \dots\dots\dots$

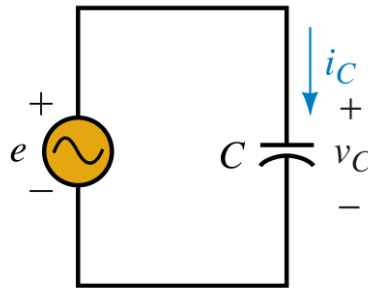

25. What is the reactance of a 5- $\mu$ F capacitor at
  - a. 60 Hz
  - b. 1000 Hz
  - c. 500 rad/s
26. For the figure of problem (24),  $e = 100 \sin \omega t$  and  $C = 5$  mF. Determine  $i_C$  at
  - a. 60 Hz
  - b. 1000 Hz
  - c. 500 rad/s
27. For the figure of problem (24), let  $C = 50$  mF.
  - a. If  $v_C = 100 \sin 377t$  V, what is  $i_C$  ?
  - b. If  $i_C = 10 \sin(2\pi \times 400t - 60^\circ)$  mA, what is  $v_C$ ?
28. For the figure of problem (24), if
  - a.  $v_C = 362 \sin(\omega t - 33^\circ)$  V,  $i_C = 94 \sin(\omega t + 57^\circ)$  mA, and  $C = 2.2$  mF, what is  $f$ ?
  - b.  $i_C = 350 \sin(\omega t + 40^\circ)$  mA,  $v_C = 3.6 \sin(\omega t + \theta)$  V, and  $f = 12$  kHz, what are  $C$  and  $\theta$ ?

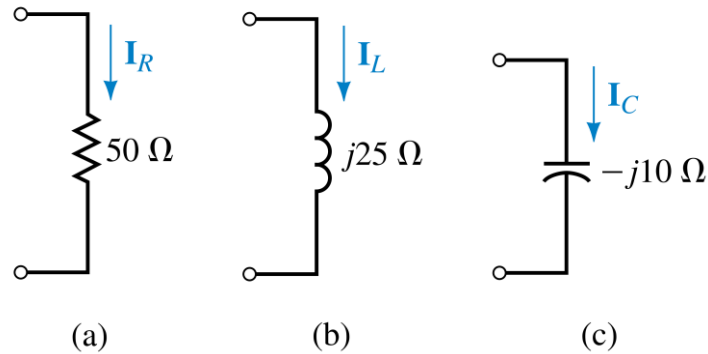29. If  $E = 100\text{V}\angle 0^\circ$  is applied across each of the circuit elements of the following figure:
- Determine each current in phasor form.
  - Express each current in time domain form



30. If the current through each circuit element of the figure of problem (29) is  $0.5\text{A}\angle 0^\circ$ :
- Determine each voltage in phasor form.
  - Express each voltage in time domain form.
31. For each of the following, determine the impedance of the circuit element and state whether it is resistive, inductive, or capacitive.
- $V = 240\text{V}\angle -30^\circ$ ,  $I = 4\text{A}\angle -30^\circ$ .
  - $V = 40\text{V}\angle 30^\circ$ ,  $I = 4\text{A}\angle -60^\circ$ .
  - $V = 60\text{V}\angle -30^\circ$ ,  $I = 4\text{A}\angle 60^\circ$ .
  - $V = 140\text{V}\angle -30^\circ$ ,  $I = 14\text{mA}\angle -120^\circ$ .
32. For each circuit of the following figure, determine the unknown.
- If  $V_L = 120\text{V}\angle 67^\circ$ ,  $L = 600\text{mH}$ , and  $f = 10\text{kHz}$ , what is  $I_L$ ?
  - If  $I_L = 48\text{mA}\angle -43^\circ$ ,  $L = 550\text{mH}$ , and  $f = 700\text{Hz}$ , what is  $V_L$ ?
  - If  $V_C = 50\text{V}\angle -36^\circ$ ,  $C = 390\text{pF}$ , and  $f = 470\text{kHz}$ , what is  $I_C$ ?
  - If  $I_C = 95\text{mA}\angle 87^\circ$ ,  $C = 6.5\text{nF}$ , and  $f = 1.2\text{MHz}$ , what is  $V_C$ ?

